

EC413

October 12, 2022

### ALUtopModule

#### EC413 Lab4

This module instantiates all other modules and has a mux to perform the various output the correct values depending on the input ALUOp. It performs the following functions:

1. MOV
2. NOT
3. Addition
4. Subtraction
5. Logical OR
6. Logical AND

The modules will all run and upon entering an ALUOp, it enters a MUX generated through case statements and outputs the value of R1. R1 then passes through the NbitReg to store the value of R1 into R0.

### Nbit\_NOT

This performs a bitwise NOT operation for each bit on the input and puts it into the output. Uses a loop to perform the action.

### NbitAdder

Creates an N-bit ripple carry adder and adds the the two inputs. It takes in inputs a, b, and c\_in and its outputs are c\_out and sum.

### NbitSub

This module takes two inputs a and b, and input c\_in = 1. It performs the bitwise NOT operation on b by calling Nbit\_NOT. It then will use the Full adder to create a ripple carry to generate the proper values. It returns c\_out and sum.

### Nbit\_OR

This performs a bitwise OR operation between inputs inval1 and inval2. It does this in a loop using the generate function and an or gate and stores the output in outval.

### Nbit\_AND

This performs a bitwise AND operation between inputs inval1 and inval2. It does this in a loop using the generate function and an and gate and stores the output in outval.

### NbitReg

Uses a D Flip-Flop to store the value of the input inval into the output outval. The ALU uses this to store the value of R1 into the register R0.

### Overall Design Hierarchy:

1. ALUtopModule
  - a. Nbit\_NOT
  - b. NbitAdder
    - i. FA\_str
  - c. NbitSub
    - i. Nbit\_NOT
    - ii. FA\_str
  - d. Nbit\_OR
  - e. Nbit\_AND
  - f. NbitReg
    - i. Dff

### ALU Operations:

ALUOp	Function
3'b000	MOV
3'b001	NOT
3'b010	ADD
3'b011	SUB
3'b100	OR
3'b101	AND
3'b110	SLT





